



Manarat International University (MIU)

Department of CSE (Evening)

Digital Logic Design (CSE-209)

Assignment 1

Due Date: 07/07/2017

Total Point: 20

Problem 1 (1 point)

Show the following operations using 2s complement:

a. $10000111 - 1011001$

b. $1011001 - 10000111$

c. $0.1001 - 0.0101$

d. $0.0101 - 0.1001$

Problem 2 (1 point)

Determine by means of a truth table the validity of DeMorgan's theorem for three variables: $(ABC)' = A' + B' + C'$.

Problem 3 (2 points)

Simplify the following expressions using Boolean algebra.

a. $AB + A(CD + CD')$

b. $(BC' + A'D)(AB' + CD')$

Problem 4 (2 points)

Given the Boolean expression $F = x'y + xyz'$:

a. Derive an algebraic expression for the complement F' .

b. Show that $F \cdot F' = 0$.

Problem 5 (2 points)

Simplify the following Boolean functions, using 3-variable maps:

a. $F(x, y, z) = \Sigma(0, 2, 6, 7)$

b. $F(A, B, C) = \Sigma(0, 2, 3, 4, 6)$

Problem 6 (2 points)

Simplify the following Boolean functions, using 4-variable maps:

a. $w'z + xz + x'y + wx'z$

b. $wxy + yz + xy'z + x'y$

Problem 7 (2 points)

Simplify the following Boolean function F, together with the don't-care conditions d, and then express the simplified function in sum of minterms:

a. $F(x,y,z) = \Sigma (0,1,2,4,5)$, $d(x,y,z) = \Sigma (3,6,7)$

b. $F(A,B,C,D) = \Sigma (1,3,5,7,9,15)$, $d(A,B,C,D) = \Sigma (4,6,12,13)$

Problem 8 (3 points)

Given the Boolean function $F = xy'z + x'y'z + xyz$

a. Simplify the function using Boolean algebra

b. List the truth table of the simplified function

c. Draw the logic diagram of the simplified function using only 2-input NAND gates.

Problem 9 (2 points)

Implement the following Boolean function together with the don't-care conditions d, using no more than three NOR gates:

$F(A,B,C,D) = \Sigma (0,1,9,11)$

$d(A,B,C,D) = \Sigma (2,8,10,14,15)$

Problem 10 (3 points)

Derive the circuits for a three-bit parity generator and four-bit parity checker using odd parity bit.