

Manarat International University (MIU)

Department of Computer Science and Engineering (Evening)

Midterm Examination (Summer 2017)

Course Code: CSE-209

Course Title: Digital Logic Design

Full Marks: 20

Time: 1 Hour 30 Minutes

Answer any 5 (five) question. All questions are of equal value.

1. Define the following terms [1 X 4 = 4]
 - a. Power Dissipation
 - b. Propagation Delay
 - c. Priority Encoder
 - d. Noise Margin

2.
 - a. Implement $F(A, B, C) = A + B'C$ as a sum of minterms.
 - b. Convert $F(X, Y, Z) = X + X'Y'$ as a product of maxterms.[2 X 2 = 4]

3. Simplify the following expressions using Boolean algebra. [2 X 2 = 4]
 - a. $AB + A(CD + CD')$
 - b. $(BC' + A'D)(AB' + CD')$

4. Implement the following Boolean function together with the don't-care conditions d, using no more than three NOR gates: [4]
$$F(A,B,C,D) = \Sigma (0,1,9,11)$$
$$d(A,B,C,D) = \Sigma (2,8,10,14,15)$$

5. Design a Decimal-to-BCD encoder. Write down the truth table and draw the circuit diagram. [4]

6. Derive the circuits for a three-bit parity generator and four-bit parity checker using odd parity bit. [2 X 2 = 4]